

ELEC5508
Assignment #2
Due: March 7 , 2006

Q1: Consider the circuit shown in Figure 1

- a) Use your MNA program to plot the magnitude of the output response in the frequency range 10KHz-10MHz. Use log-log scale.
 - Use AWE of order $[1/2]$ with a suitable scaling factor to approximate the output response and compare with your results obtained in part a.
 - Find the dominant poles.
 - Find the time-domain response corresponding to a 10mA ideal step input.
 - Find the time-domain response corresponding to a 10mA step input with rise time=1 μ S. Compare your results with HSPICE (or equivalent).
- C) Repeat part b using AWE of order $[2/3]$ and order $[3/4]$

Q2: Consider the circuit shown in Figure 2

- a) Use your MNA program to plot the magnitude of the output response in the frequency range 10KHz-10GHz. Use log-log scale.
 - Use AWE of order $[1/2]$ with a suitable scaling factor to approximate the output response and compare with your results obtained in part a.
 - Find the dominant poles.
 - Find the time-domain response corresponding to a 5V ideal step input.
 - Find the time-domain response corresponding to a 5V step input with rise-time= 1nS. Compare your results with HSPICE (or equivalent).
 - Find the time-domain response corresponding to a 5V pulse with rise/fall time=1nS and pulse width=12nS. Compare your results with HSPICE (or equivalent).
- C) Repeat part b using AWE of order $[2/3]$ and order $[3/4]$

All capacitors are 10nF
 $R1=50\text{ Ohms}$
 $R=10\text{ Ohms}$

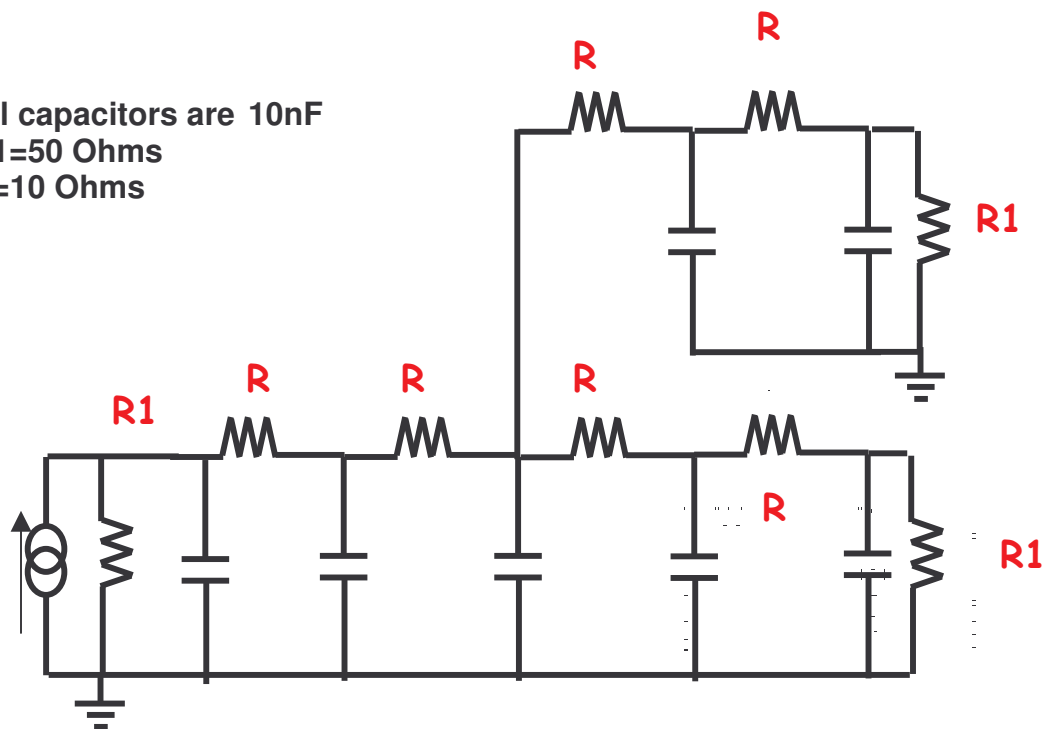


Figure 1

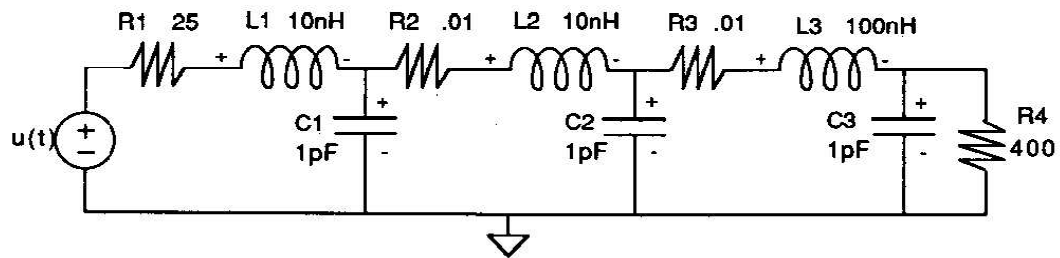


Figure 2